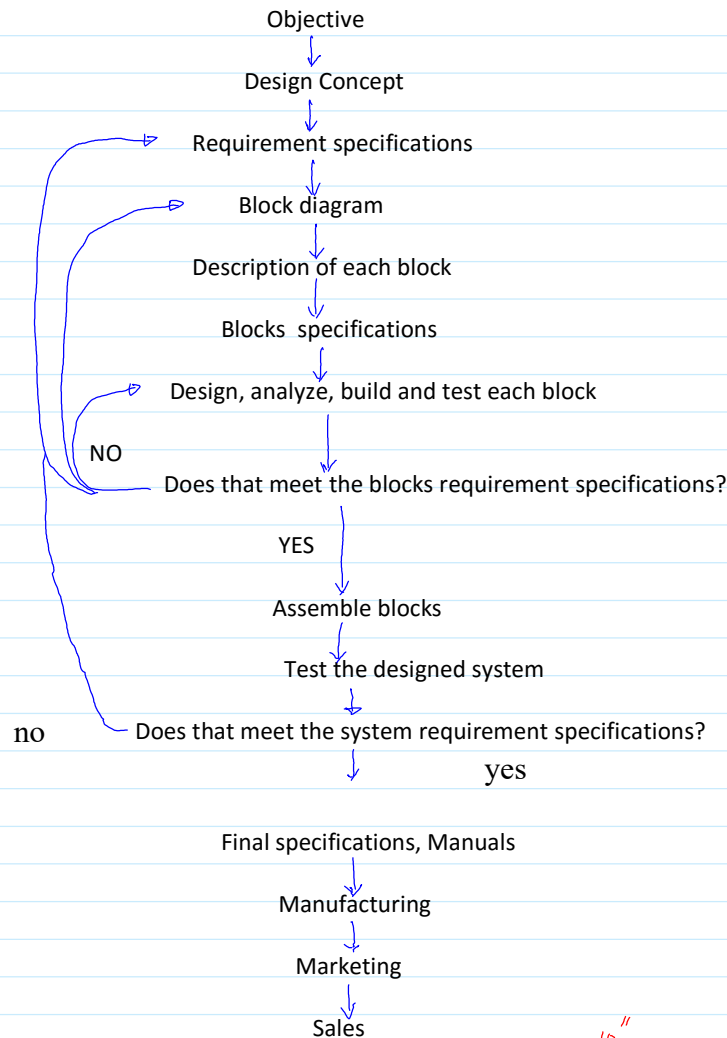


Lab2: Design, implement and test a 120Vac to +5Vdc supply with indicators and a USB connector for a cell phone/MP3 player charging.

To be used a power supply for the emergency light system.

→ **Emergency light system design:**

Design Steps:




Objective: An emergency light for home use


Initial Design Concept: →

Requirement Specifications:

- size 6" x 4" x 10"
- 120V, 5V (USB), 10w bulb, 7Ahv Battery
- 4 indicators
- test input, light sensor

System Block Diagram:

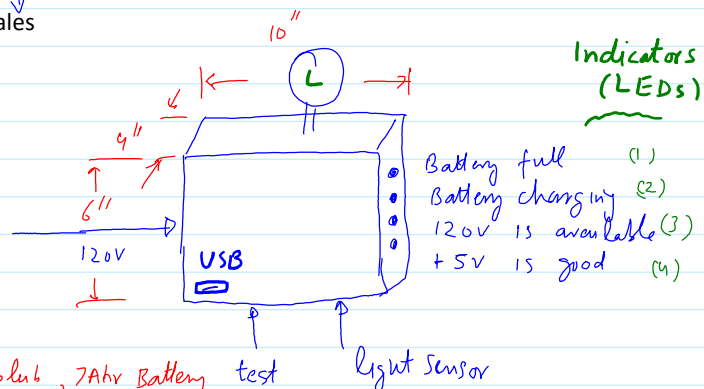

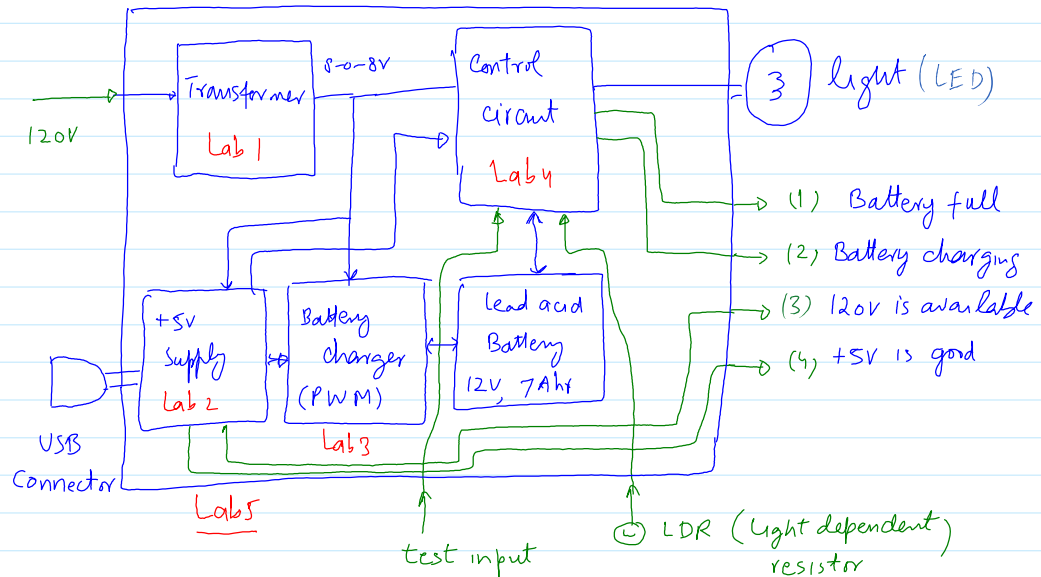

List specs of each block, design each block, test each block, assemble the system. Improve / fix issues as needed.


Lab2: Design, implement and test a 120Vac to +5Vdc supply with indicators and a USB connector for a cell phone/MP3 player charging.

Introduction to USB (Universal serial Bus)


USB 1.1, USB 2.0, USB 3.0, USB 3.1

Black Connector

Blue Connector

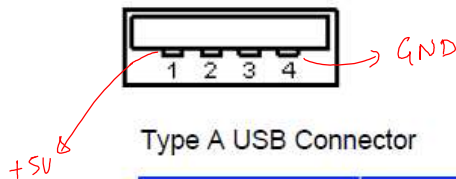

Type A USB Connector

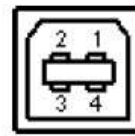

Type B USB Connector

Pin Number	Cable Colour	Function
1	Red	V _{BUS} (5 volts)
2	White	D-
3	Green	D+
4	Black	Ground

USB Yellow connector

→ always on
(supplies power even when computer is in sleep mode.)
→ used for charging.



The receiver defines a differential '1' as D+ 200mV greater than D- and a differential '0' as D+ 200mV less than D-

There are three classes of USB functions,

- Low-power bus powered functions (100mA, 4.40V to 5.25V) Thumb drives
- High-power bus powered functions (100mA initially (configuration), but 500mA later, 4.75 - 5.25V range) MP3 Players
- Self-powered functions (100mA from the bus, remaining from its own power source) External HD, FD, DVD etc.

USB 3.0 → 900mA, 5Gb/s (USB 2.0 480 Mb/s)
USB 3.1 → upto 5A (for charging) 10Gb/s speed



Apple USB Power Adapter


Input: 100-240V · 0.2A 50-60Hz · Output: 5V up to 1.0A

(Based on a switched mode power supply)



Other products

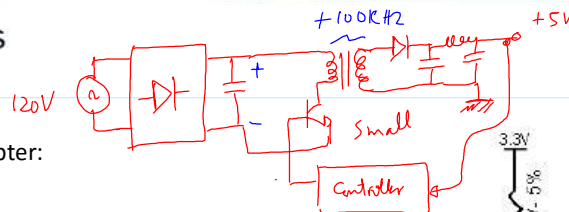
Typical circuit in a switching power adapter:




A USB device must indicate its speed by pulling either the D+ or D- line high to 3.3 volts. A full speed device, pictured below will use a pull up resistor attached to D+ to specify itself as a full speed device.

These pull up resistors at the device end will also be used by the host or hub to detect the presence of a device connected to its port. Without a pull up resistor, USB assumes there is nothing connected to the bus. Some devices have this resistor built into its silicon, which can be turned on and off under firmware control, others require an external resistor.

Connect 15k resistors on charger Side. (D+ and D- to GND)

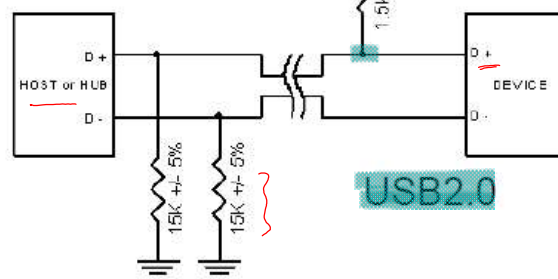

USB2.0

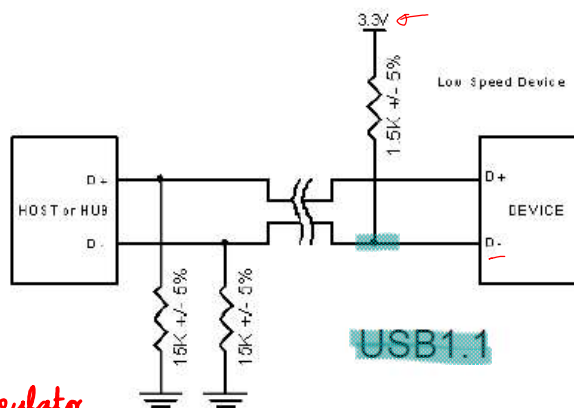

USB1.1

How to get a stable +5V supply?

→ use a fixed voltage regulator

LM78xx ; LM79xx

LM7812 → 12V

Absolute Maximum Ratings

Parameter	Symbol	Value	Unit
Input Voltage (for $V_O = 5V$ to $18V$)	V_I	35	V
(for $V_O = 24V$)	V_I	40	V
Thermal Resistance Junction-Cases (TO-220)	$R_{\theta JC}$	5	$^{\circ}C/W$
Thermal Resistance Junction-Air (TO-220)	$R_{\theta JA}$	65	$^{\circ}C/W$
Operating Temperature Range	$TOPR$	$0 \sim +125$	$^{\circ}C$



LM7805

Up to 1A output current

Absolute Maximum Ratings

LM 101

Parameter	Symbol	Value	Unit
Input Voltage (for $V_O = 5V$ to $18V$) (for $V_O = 24V$)	V_I V_{VI}	35 40	V
Thermal Resistance Junction-Cases (TO-220)	$R_{\theta JC}$	5	$^{\circ}C/W$
Thermal Resistance Junction-Air (TO-220)	$R_{\theta JA}$	65	$^{\circ}C/W$
Operating Temperature Range	$TOPR$	$0 \sim +125$	$^{\circ}C$
Storage Temperature Range	$TSTG$	$-65 \sim +150$	$^{\circ}C$



LM7805

Up to 1A output current

LM7905 $\rightarrow -5V$

LM7824 $\rightarrow 24V$

LM7809 $\rightarrow 9V$

Electrical Characteristics (MC7805/LM7805)

(Refer to test circuit, $0^{\circ}C < T_J < 125^{\circ}C$, $I_O = 500mA$, $V_I = 10V$, $C_I = 0.33\mu F$, $C_O = 0.1\mu F$, unless otherwise specified)



Parameter	Symbol	Conditions	MC7805/LM7805			Unit
			Min.	Typ.	Max.	
Output Voltage	V_O	$T_J = +25^{\circ}C$	4.8	5.0	5.2	V
		$5.0mA \leq I_O \leq 1.0A$, $P_O \leq 15W$ $V_I = 7V$ to $20V$	4.75	5.0	5.25	
Line Regulation (Note1)	Regline	$T_J = +25^{\circ}C$	-	$V_O = 7V$ to $25V$	4.0	mV
				$V_I = 8V$ to $12V$	1.6	
Load Regulation (Note1)	Regload	$T_J = +25^{\circ}C$	-	$I_O = 5.0mA$ to $1.5A$	9	mV
				$I_O = 250mA$ to $750mA$	4	
Quiescent Current	I_Q	$T_J = +25^{\circ}C$	-	5.0	8.0	mA
Quiescent Current Change	ΔI_Q	$I_O = 5mA$ to $1.0A$	-	0.03	0.5	mA
		$V_I = 7V$ to $25V$	-	0.3	1.3	
Output Voltage Drift	$\Delta V_O / \Delta T$	$I_O = 5mA$	-	-0.8	-	mV/ $^{\circ}C$




LM7805

Up to 100mA output

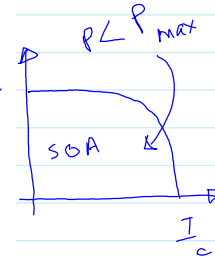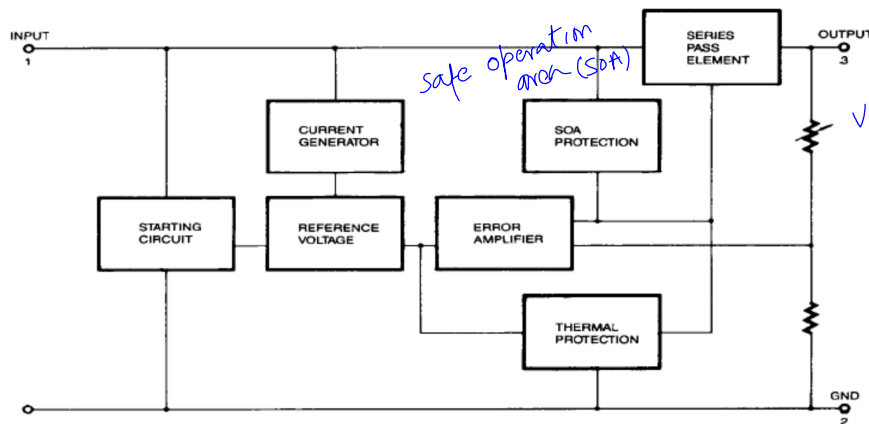Internal Block Diagram (Fixed voltage regulator)



Circuit for Lab2


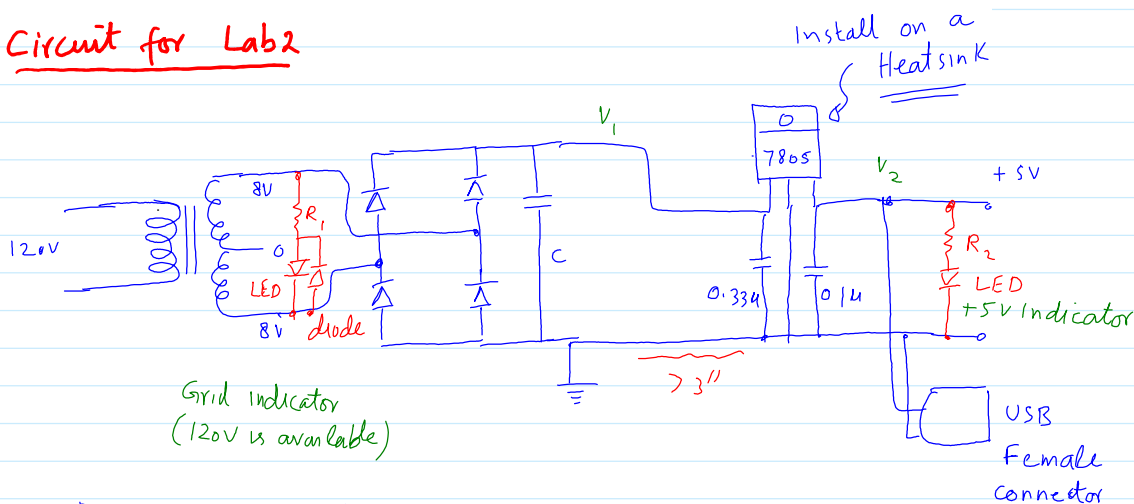


Design: C , R_1 , R_2 , diodes?

$$12V - 1.4V = V_{in}$$

Design: C, R_1, R_2 , diodes?


transformer (8V-0-8V)
output

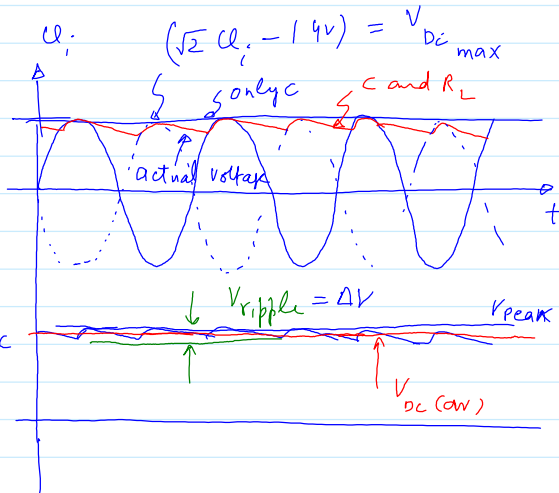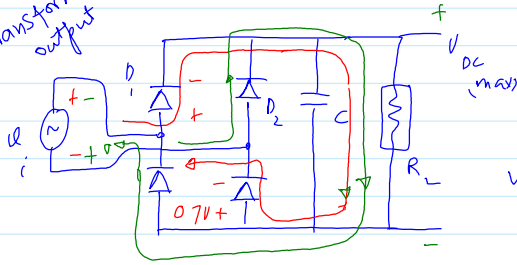

Eng 4854

$$C = \frac{V_{max} \Delta V}{2 f_i \Delta V R_L}$$

$$\eta = 80\%$$

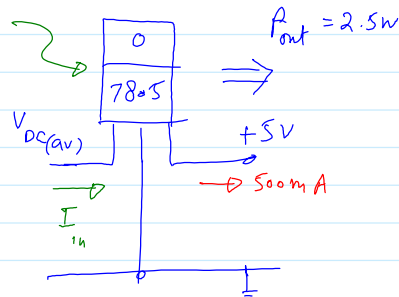

$$V_{max} = \sqrt{2} (16) - 1.4V = 21.22V$$

$$\Delta V = \text{ripple voltage} = 0.5V \text{ (assume)}$$

$$V_{DC(av)} = 21.22 - \frac{0.5}{2} = 20.97V$$

USB 2.0 ; 500mA, 5V

$$P_{out} = 2.5W$$

say $\eta = 80\%$

$$I_{in} = \frac{(2.5)}{(0.8) V_{DC(av)}} = \frac{2.5}{0.8 \times 20.97} = 0.15A$$

$$R_L = \frac{V_{DC(av)}}{I_{in}} = \frac{20.97}{0.15} = 139.8 \Omega \text{ (equivalent)}$$


$$C = \frac{21.22}{2 (60) (0.5) (139.8)} = 2529 \mu F$$

use

2200 μF

35V

standard

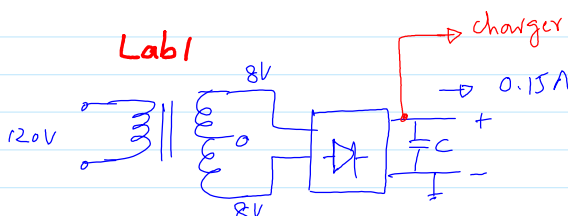

Current drawn will be higher when a charger is connected

→ ripple will increase

→ Regulator will take care of that.



$$\text{diode current} = \frac{0.15}{2} = 0.075A$$

diode current = $\frac{0.15}{2} = \underline{\underline{0.075 \text{ A}}}$ care of that.

$\text{PIV} = \sqrt{2} U_i - 0.7$ } for full bridge rectifier (Ex: 4854)

$= \sqrt{2} (16) - 0.7 = \underline{\underline{21.2 \text{ V}}}$

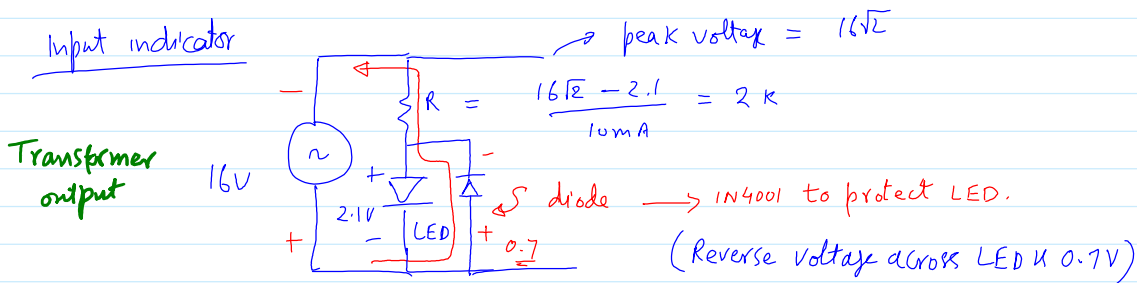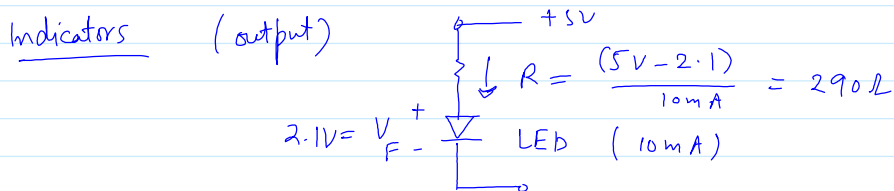
use \Rightarrow Diodes \rightarrow 56V, 1A 1N4001 (good for charger and +5V supply)



V_R for LED $\approx 5V$

Task #1: Build above shown circuit on a prototyping board. (soldering)

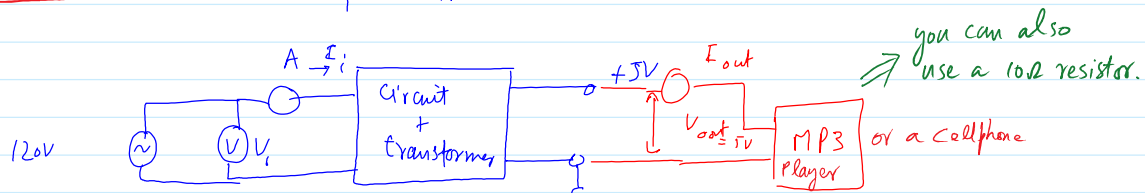Task #2: Testing #1 Find no load losses of the circuit $= \frac{V_i I_i}{V_o I_o}$



#2


#2 Find η when a MP3 player or a cell phone or a 10Ω resistor is connected as a load.

$\eta = \frac{V_o I_o}{V_i I_i}$

#3 Draw V_L and +5V waveforms when a 10Ω load is connected.

across +5V output ($V_L, \Delta V_L$) ($500mA, USB 2.0$)
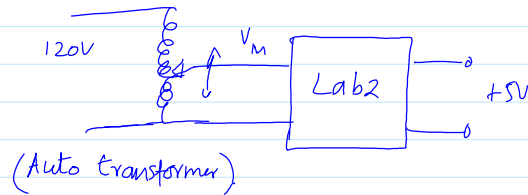
#4 Find $V_{in(min)}$ for proper operation (+5V output)



#5 Find No load and loaded power factor




Warning



DO NOT CONNECT PROBE DIRECTLY TO LINE. USE TRANSFORMER LOW VOLTAGE SIDE.



Current probe

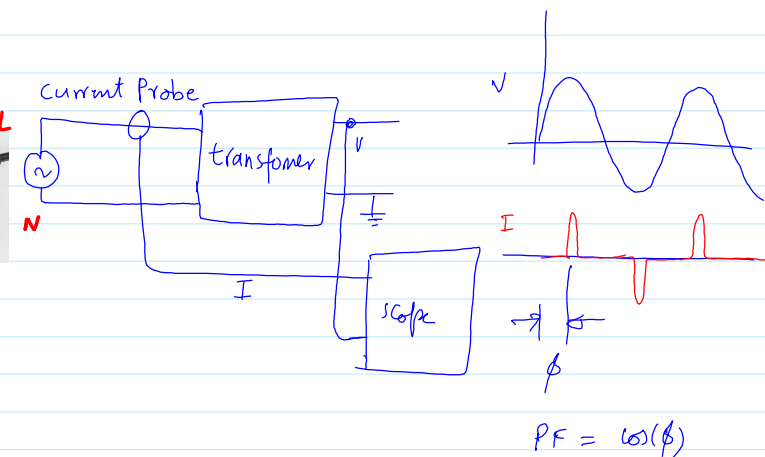

#6 Find energy consumed in a year (no load operation)

$$= V_{in} I_{in} \times 8760$$

#7 Compare result #6 with the result of a commercial adapter

(your η may be low since charger part was ignored)

(most of the transformer output current will go to PWM charger)